

1. Write a Verilog code for D Flip-Flop with synchronous and asynchronous reset and verify its functionality using test bench. Synthesize the design, tabulate the area, power and timing report.


**Tools required:**

- Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)
- Synthesis: Genus

**D Flip-Flop:** A D (or Delay) Flip Flop is a digital electronic circuit used to delay the change of state of its output signal ( $Q$ ) until the next rising edge of a clock timing input signal occurs. The D Flip Flop acts as an electronic memory component since the output remains constant unless deliberately changed by altering the state of the D input followed by a rising clock signal.

**a) D Flip-Flop with synchronous reset:**

 **D Flip-Flop with synchronous reset block diagram:**



**D Flip-Flop with synchronous reset truth table:**

rst	clk	d	q	qb
1	↑	X	0	1
0	↑	0	0	1
0	↑	1	1	0
1	↑	X	0	1

**Verilog Code for D Flip-Flop with synchronous reset:**

```
module d_ff (q, qb, d, clk, rst);
output reg q;
output qb;
```

```
input d, clk, rst;
```

```
always @(posedge clk)
```

```
begin
```

```
if (rst)
```

```
q = 0;
```

```
else
```

```
q = d;
```

```
end
```

```
assign qb = ~q;
```

```
endmodule
```

***Testbench for D Flip-Flop with synchronous reset module:***

```
module d_ff_test;
```

```
reg clk, rst, d;
```

```
wire q, qb;
```

```
d_ff d1(q, qb, d, clk, rst);
```

```
initial
```

```
begin
```

```
$monitor ("time = %0d", $time, "ns", "rst =", rst, "d =", d, "q =", q, "qb =", qb);
```

```
#40 $finish;
```

```
end
```

```
initial
```

```
clk = 0;
```

```
always
```

```
#5 clk = ~clk;
```

```
initial
begin
rst = 1; d = 0;
#10 rst = 0;
#10 d = 1;
#10 rst = 1;
end

endmodule
```

**Result:**

Non-GUI Output:

GUI Output:

Area Report

Power Report


Gates Report:

Timing Report:

Schematic:

***b) D Flip-Flop with asynchronous reset:***

 ***D Flip-Flop with asynchronous reset block diagram:***



***D Flip-Flop with synchronous reset truth table:***

rst	clk	d	q	qb
0	X	X	0	1
1	↑	0	0	1
1	↑	1	1	0
0	X	X	0	1

***Verilog Code for D Flip-Flop with asynchronous reset:***

```

module dff (q, qb, d, clk, rst);
output reg q;
output qb;
input d, clk, rst;

always @(posedge clk, negedge rst)

begin
if (!rst)
q = 0;
else
q = d;
end

assign qb = ~q;

endmodule

```

***Testbench for D Flip-Flop with asynchronous reset module:***

```

module dff_test;

```

```
reg d, rst, clk;
wire q, qb;
dff d1 (q, qb, d, clk, rst);
initial
begin
$monitor ("time=%0d", $time, "ns", "rst =", rst, "d =", d, "q =", q, "qb =", qb);
#40 $finish;
end

initial
begin
d = 0;
clk = 0;
end

always
#5 clk = ~clk;

initial
begin
rst = 0;
#10 rst = 1;
#10 d = 1;
#10 rst = 0;
end

endmodule
```

**Result:**

Non-GUI Output:

GUI Output:

Area Report

Power Report



*Gates Report:*

*Timing Report:*

Schematic:

- 2. Write a Verilog code for SR Flip-Flop with synchronous and asynchronous reset and verify its functionality using test bench. Synthesize the design, tabulate the area, power and timing report.**


***Tools required:***

- *Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)*
- *Synthesis: Genus*

**SR Flip-Flop:** The SR flip flop is a 1-bit memory bistable device having two inputs, i.e., SET and RESET. The SET input 's' set the device or produce the output 1, and the RESET input 'r' reset the device or produce the output 0. The SET and RESET inputs are labelled as s and r, respectively. The SR flip flop stands for "Set-Reset" flip flop. The reset input is used to get back the flip flop to its original state from the current state with an output 'q'. This output depends on the set and reset conditions, which is either at the logic level "0" or "1".

**a) SR Flip-Flop with synchronous reset:**

 **SR Flip-Flop with synchronous reset block diagram:**



**SR Flip-Flop with synchronous reset truth table:**

rst	clk	S	r	q	qb
1	↑	X	X	0	1
0	↑	0	0	q	qb
0	↑	0	1	0	1
0	↑	1	0	1	0
0	↑	1	1	X	X

**Verilog Code for SR Flip-Flop with synchronous reset:**

```
module sr_ff (q, qb, s, r, clk, rst);
```

```
output reg q;
```

```
output qb;
```

```
input s, r, clk, rst;
```

```
always @(posedge clk)
```

```
begin
```

```
if (rst)
```

```
q = 0;
else
if (s == 0 && r == 0)
q = q;
else
if (s == 0 && r == 1)
q = 0;
else
if (s == 1 && r == 0)
q = 1;
else
if (s == 1 && r == 1)
q = 1'b0;
end
assign qb = ~q;

endmodule
```

***Testbench for SR Flip-Flop with synchronous reset module:***

```
module sr_ff_test;
reg s, r, clk, rst;
wire q, qb;

sr_ff s1(q, qb, s, r, clk, rst);

initial
begin
$monitor ("time = %0d", $time, "ns", "s =", s, "r =", r, "rst =", rst, "q =", q, "qb =", qb);
#80 $finish;
end

initial
clk = 1'b0;
```

```
always
#5 clk = ~clk;

initial
begin
rst = 1; s = 1; r = 0;
#10; rst = 0;
#10; s = 0; r = 0;
#10; s = 0; r = 1;
#10; s = 1; r = 0;
#10; s = 1; r = 1;
#10; s = 1; r = 0;
#10; rst = 1;
end
endmodule
```

**Result:**

Non-GUI Output:

GUI Output:

Area Report

Power Report


*Gates Report:*

*Timing Report:*

Schematic:

***b) SR Flip-Flop with asynchronous reset:***

 ***SR Flip-Flop with asynchronous reset block diagram:***



***SR Flip-Flop with asynchronous reset truth table:***

rst	clk	S	r	q	qb
0	X	X	X	0	1



1	↑	0	0	q	qb
1	↑	0	1	0	1
1	↑	1	0	1	0
1	↑	1	1	X	X

***Verilog Code for SR Flip-Flop with asynchronous reset:***

```

module srff (q, qb, s, r, clk, rst);
output reg q;
output qb;
input s, r, clk, rst;

always @(posedge clk, negedge rst)

begin
if (!rst)
q = 0;
else
if (s == 0 && r == 0)
q = q;
else
if (s == 0 && r == 1)
q = 0;
else
if (s == 1 && r == 0)
q = 1;
else
if (s == 1 && r == 1)
q = 1'bx;
end

assign qb = ~q;

endmodule

```

***Testbench for SR Flip-Flop with asynchronous reset module:***

```
module srff_test;
reg s, r, clk, rst;
wire q, qb;

srff s1(q, qb, s, r, clk, rst);

initial
begin
$monitor ("time = %0d", $time, "ns", "s =", s, "r =", r, "rst =", rst, "q =", q, "qb =", qb);
#80 $finish;
end

initial
clk = 1'b0;

always
#5 clk = ~clk;

initial
begin
rst = 0; s = 1; r = 0;
#10; rst = 1;
#10; s = 0; r = 0;
#10; s = 0; r = 1;
#10; s = 1; r = 0;
#10; s = 1; r = 1;
#10; s = 1; r = 0;
#10; rst = 0;
end

endmodule
```

**Result:**

Non-GUI Output:

GUI Output:

Area Report

Power Report

*Gates Report:*

*Timing Report:*

Schematic:

**3. Write a Verilog code for JK Flip-Flop with synchronous and asynchronous reset and verify its functionality using test bench. Synthesize the design, tabulate the area, power and timing report.**


***Tools required:***

- *Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)*
- *Synthesis: Genus*

***JK Flip-Flop:*** The JK flip-flop is the most versatile of the basic flip flops. A JK flip-flop is used in clocked sequential logic circuits to store one bit of data. It is almost identical in function to an SR flip flop. The only difference is eliminating the undefined state where both S and R are 1. Due to this additional clocked input, a JK flip-flop has four possible input combinations, such as "logic 1", "logic 0", "no change" and "toggle".

***a) JK Flip-Flop with synchronous reset:***

 ***JK Flip-Flop with synchronous reset block diagram:***



***JK Flip-Flop with synchronous reset truth table:***

rst	clk	J	k	q	qb
1	↑	X	X	0	1
0	↑	0	0	q	qb
0	↑	0	1	0	1
0	↑	1	0	1	0
0	↑	1	1	~q	~qb

***Verilog Code for JK Flip-Flop with synchronous reset:***

```
module jk_ff (q, qb, j, k, clk, rst);
```

```
output reg q;
```

```
output qb;
```

```
input j, k, clk, rst;
```

```
always @(posedge clk)
```

```
begin
```

```
if (rst)
```

```
q = 0;
```

```
else
```

```
if (j == 0 && k == 0)
```

```
q = q;
```

```
else
```

```
if (j == 0 && k == 1)
```

```
q = 0;
```

```
else
```

```
if (j == 1 && k == 0)
```

```
q = 1;
```

```
else
```

```
if (j == 1 && k == 1)
```

```
q = ~q;
```

```
end
```

```
assign qb = ~q;
```

```
endmodule
```

***Testbench for JK Flip-Flop with synchronous reset module:***

```
module jk_ff_test;
```

```
reg j, k, clk, rst;
```

```
wire q, qb;
```

```
jk_ff j1(q, qb, j, k, clk, rst);
```

```
initial
```

```
begin
```

```
$monitor ("time = %0d", $time, "ns", "j =", j, "k =", k, "rst =", rst, "q =", q, "qb =", qb);
```

```
#80 $finish;
```

```
end
```

```
initial
```

```
clk = 1'b0;
```

```
always
```

```
#5 clk = ~clk;
```

```
initial
```

```
begin
```

```
rst = 1; j = 1; k = 0;
```

```
#10; rst = 0;
```

```
#10; j = 0; k = 0;
```

```
#10; j = 0; k = 1;
```

```
#10; j = 1; k = 0;
```

```
#10; j = 1; k = 1;  
#10; j = 1; k = 0;  
#10; rst = 1;  
end  
endmodule
```

**Result:**

Non-GUI Output:

GUI Output:

Area Report



*Power Report*


*Gates Report:*

*Timing Report:*

Schematic:

***b) JK Flip-Flop with asynchronous reset:***

 ***JK Flip-Flop with asynchronous reset block diagram:***



***JK Flip-Flop with asynchronous reset truth table:***

rst	clk	J	k	q	qb
0	X	X	X	0	1
1	↑	0	0	q	qb
1	↑	0	1	0	1
1	↑	1	0	1	0
1	↑	1	1	~q	~qb

***Verilog Code for JK Flip-Flop with asynchronous reset:***

```

module jkff (q, qb, j, k, clk, rst);
output reg q;
output qb;
input j, k, clk, rst;

```

```
always @(posedge clk, negedge rst)
```

```
begin
```

```
if (!rst)
```

```
q = 0;
```

```
else
```

```
if (j == 0 && k == 0)
```

```
q = q;
```

```
else
```

```
if (j == 0 && k == 1)
```

```
q = 0;
```

```
else
```

```
if (j == 1 && k == 0)
```

```
q = 1;
```

```
else
```

```
if (j == 1 && k == 1)
```

```
q = ~q;
```

```
end
```

```
assign qb = ~q;
```

```
endmodule
```

***Testbench for JK Flip-Flop with asynchronous reset module:***

```
module jkff_test;
```

```
reg j, k, clk, rst;
```

```
wire q, qb;
```

```
jkff j1(q, qb, j, k, clk, rst);
```

```
initial
```

```
begin
```

```
$monitor ("time = %0d", $time, "ns", "j =", j, "k =", k, "rst =", rst, "q =", q, "qb =", qb);  
#80 $finish;  
end
```

```
initial  
clk = 1'b0;  
  
always  
#5 clk = ~clk;  
initial  
begin  
rst = 0; j = 1; k = 0;  
#10; rst = 1;  
#10; j = 0; k = 0;  
#10; j = 0; k = 1;  
#10; j = 1; k = 0;  
#10; j = 1; k = 1;  
#10; j = 1; k = 0;  
#10; rst = 0;  
  
end  
  
endmodule
```

**Result:**

Non-GUI Output:

GUI Output:

Area Report

Power Report

*Gates Report:*

*Timing Report:*

Schematic:



4. Write Verilog code for 32-bit ALU supporting four logical and four arithmetic operations, use case statement and if statement for ALU behavioral modeling.
  - a. Perform functional verification using test bench.
  - b. Synthesize the design targeting suitable library by setting area and timing constraints.
  - c. For various constraints set, tabulate the area, power and delay for the synthesized netlist.
  - d. Identify the critical path and set the constraints to obtain optimum gate level netlist with suitable constraints.


Compare the synthesize results of ALU modeled using if and case statements.

***Tools required:***

- *Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)*
- *Synthesis: Genus*

***Arithmetic Logical Unit (ALU):*** ALU is the fundamental building block of the processor, which is responsible for carrying out the arithmetic and logical functions. ALU comprises of combinational logic that implements arithmetic operations such as addition, subtraction, multiplication, division etc., and logical operations such as AND, OR, NAND, NOR etc.,. The ALU reads two input operands *a* and *b*. The operation to perform on these input operands is selected using control input *sel*. The ALU performs the selected operation on the input operands *a* and *b* and produces the output *alu\_out*.

 ***Arithmetic Logical Unit (ALU) block diagram:***



**Arithmetic Logical Unit (ALU) truth table:**

a	b	sel	operation	alu_out
32'h FEDCBA98	32'h 89ABCDEF	0	Addition	64'h 00000001_88888887
		1	Subtraction	64'h 00000000_7530ECA9
		2	Multiplication	64'h 890F2A50_AD05EBE8
		3	Division	64'h 00000000_00000001
		4	AND	64'h 00000000_88888888
		5	OR	64'h 00000000_FFFFFFFF
		6	XOR	64'h 00000000_77777777
		7	XNOR	64'h FFFFFFFF_88888888

**a) 32-bit ALU using case statement:**

**Verilog code for 32-bit ALU using case statement:**

```

module alu (a, b, sel, alu_out);
input [31:0] a, b;
input [2:0] sel;
output reg [63:0] alu_out;
always @ (*)
begin
case (sel)
3'b000: alu_out = a + b;
3'b001: alu_out = a - b;
3'b010: alu_out = a * b;
3'b011: alu_out = a / b;

```

```

3'b100: alu_out = a & b;
3'b101: alu_out = a | b;
3'b110: alu_out = a ^ b;
3'b111: alu_out = ~(a ^ b);
default;;
endcase
end
endmodule

```

***Testbench for 32-bit ALU using case statement:***

```

module alu_test;
reg [31:0] a, b;
reg [2:0] sel;
wire [63:0] alu_out;

alu a1 (a, b, sel, alu_out);

initial
begin
a = 32'hFEDCBA98;
b = 32'h89ABCDEF;
sel = 3'b000;
$monitor ("a = 0x%0h b = 0x%0h sel = 0x%0h alu_out = 0x%0h", a, b, sel, alu_out);
#80; $finish;
end
always
#10 sel = sel + 3'b001;
endmodule

```

**Creating an SDC File:**

➤ In terminal type “gedit alu\_top.sdc” to create an SDC file.

```

set_input_delay -max 0.2 [get_ports "a"]
set_input_delay -max 0.25 [get_ports "b"]

```

```
set_output_delay -max 0.2 [get_ports "alu_out"]
```

**Performing Synthesize:**

The following are commands to perform synthesize

```
genus -gui
```

```
read_lib /home/install/cad/slow.lib
```

```
read_hdl alu.v
```

```
elaborate
```

```
read_sdc alu_top.sdc
```

```
set_db syn_generic_effort medium
```

```
set_db syn_map_effort medium
```

```
set_db syn_opt_effort medium
```

```
syn_generic
```

```
syn_map
```

```
syn_opt
```

```
write_hdl > alu_netlist.v
```

```
write_sdc > alu_top.sdc
```

```
report_power
```

```
report_gates
```

```
report_timing
```

```
report_area
```

```
report_qor -levels_of_logic -power -exclude_constant_nets
```

**Result:**

Non-GUI output:

GUI Output:

Area report:

Power report:

*Gates Report:*

*Timing report:*

Schematic:

***b) 32-bit ALU using if statement:***

***Verilog code for 32-bit ALU using if statement:***

```
module alu (a, b, sel, alu_out);  
input [31:0] a, b;  
input [2:0] sel;  
output reg [63:0] alu_out;  
always @ (*)  
begin  
if (sel == 3'b000)  
alu_out = a + b;  
else if (sel == 3'b001)
```

```
alu_out = a - b;
else if (sel == 3'b010)
alu_out = a * b;
else if (sel == 3'b011)
alu_out = a / b;
else if (sel == 3'b100)
alu_out = a & b;
else if (sel == 3'b101)
alu_out = a | b;
else if (sel == 3'b110)
alu_out = a ^ b;
else
alu_out = ~(a ^ b);
end
endmodule
```

***Testbench for 32-bit ALU using if statement:***

```
module alu_test;
reg [31:0] a, b;
reg [2:0] sel;
wire [63:0] alu_out;
alu a1 (a, b, sel, alu_out);

initial
begin
a = 32'hFEDCBA98;
b = 32'h89ABCDEF;
sel = 3'b000;
$monitor ("a = 0x%0h b = 0x%0h sel = 0x%0h alu_out = 0x%0h", a, b, sel, alu_out);
#80; $finish;
end

always
```



```
#10 sel = sel + 3'b001;
```

```
endmodule
```

**Result:**

Non-GUI output:

GUI Output:

Area report:

Power report:

Gates Report:

Timing report:

Schematic:


***\*\*Compare the results of 32-bit ALU case statement and 32-bit ALU using if statement\*\****

5. Write Verilog code for 4-bit shift and add multiplier and carry out the following:
  - a. Verify the functionality using test bench
  - b. Synthesize the design by setting proper constraints and obtain the gate level netlist From the report generated identify Critical path, Maximum delay, Total number of cells, Power requirement and Total area required.

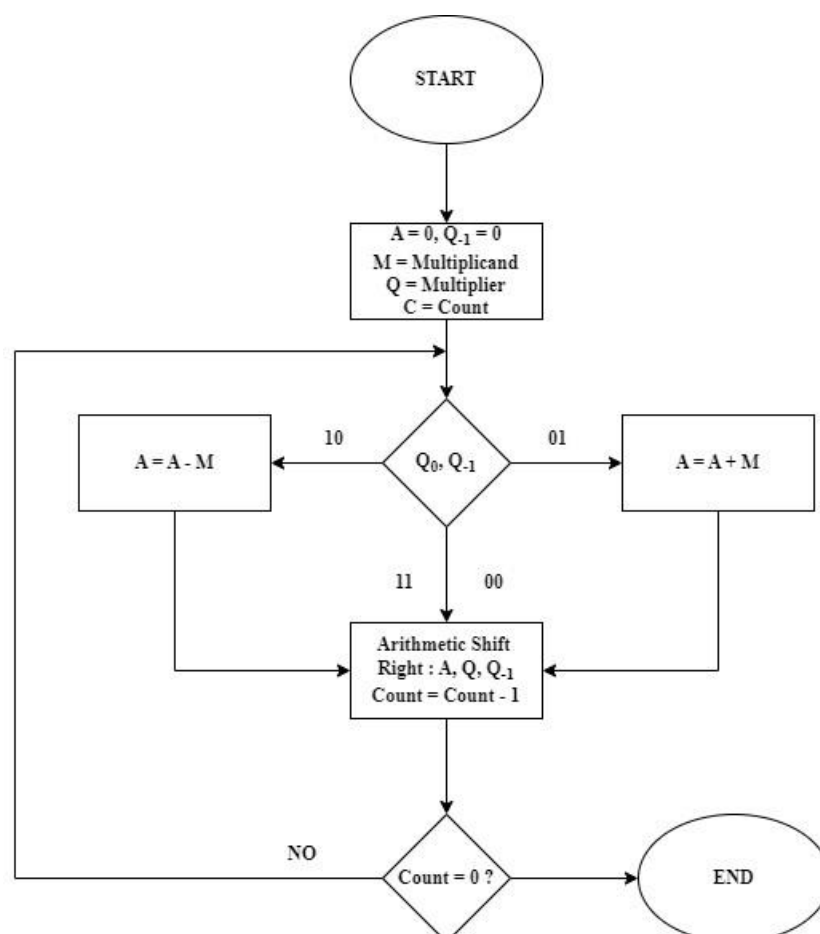**Tools required:**


- Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)
- Synthesis: Genus

**4-bit shift and add multiplier** is one which multiplies 2 signed integers in 2's complement. This is depicted in the following figure with a brief description. This approach uses fewer additions and subtractions than more straightforward algorithms.



The multiplicand and multiplier are placed in the  $m$  and  $Q$  registers respectively. A 1-bit register is placed logically to the right of the LSB (least significant bit)  $Q_0$  of  $Q$  register. This is denoted by  $Q-1$ .  $A$  and  $Q-1$  are initially set to 0. Control logic checks the two bits  $Q_0$  and  $Q-1$ . If the two bits are same (00 or 11) then all of the bits of  $A$ ,  $Q$ ,  $Q-1$  are shifted 1 bit to the right. If they are not the same and if the combination is 10 then the multiplicand is subtracted from  $A$  and if the combination is 01 then the multiplicand is added with  $A$ . In both the cases results are stored in  $A$ , and after the addition or subtraction operation,  $A$ ,  $Q$ ,  $Q-1$  are right shifted. The shifting is the arithmetic right shift operation where the left most bit namely,  $A_{n-1}$  is not only shifted into  $A_{n-2}$  but also remains in  $A_{n-1}$ . This is to preserve the sign of the number in  $A$  and  $Q$ . The result of the multiplication will appear in the  $A$  and  $Q$ .

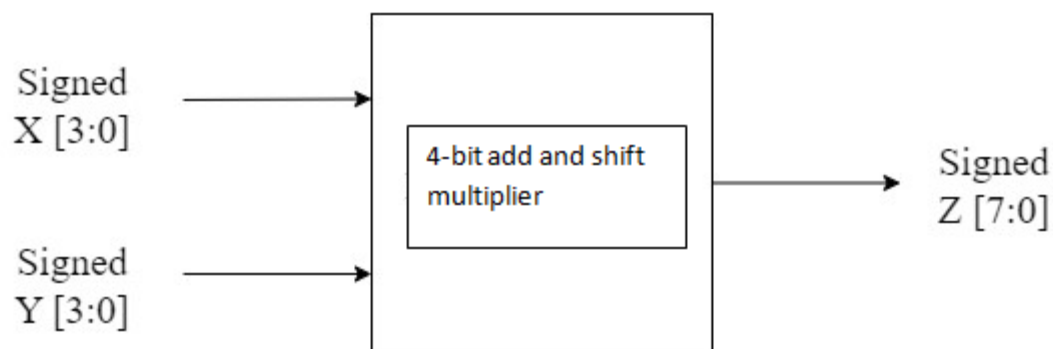**4-bit shift and add multiplier block diagram:**



***4-bit shift and add multiplier truth table:***

<b>X</b>	<b>Y</b>	<b>Z</b>
0	0	0
-5	7	-35

***Verilog code for 4-bit shift and add multiplier:***

```

module mul (X, Y, Z);
input signed [3:0] X, Y;
output signed [7:0] Z;
reg signed [7:0] Z;
reg [1:0] temp;
integer i;
reg E1;
reg [3:0] Y1;

always @ (X, Y)
begin
Z = 8'd0;
E1 = 1'd0;
for (i = 0; i < 4; i = i + 1)
begin
temp = {X[i], E1};
Y1 = - Y;

case (temp)
2'd2: Z [7 : 4] = Z [7 : 4] + Y1;
2'd1: Z [7 : 4] = Z [7 : 4] + Y;
default: begin end
endcase

Z = Z >> 1;
Z[7] = Z[6];
E1 = X[i];
end

```

```
        if (Y == 4'd8)
            begin
                Z = - Z;
            End
        end
    end
```

```
endmodule
```

***Testbench for 4-bit shift and add multiplier:***

```
module mul_tb;
    reg signed [3:0] X, Y;
    wire signed [7:0] Z;

    mul b1 (.X(X), .Y(Y), .Z(Z));

    initial
    begin

        X = 0;
        Y = 0;
        #10;
        X=-5;
        Y=7;
        #20; $finish;

    end

    initial
    $monitor($time, "X = %d", X," Y = %d",Y, "Z = %d", Z);

endmodule
```

**Result:**

Non-GUI Output:

GUI Output:

Area Report



Power Report

Gates Report:

Timing Report:

Schematic:


6) Write verilog code for 4-bit adder and verify its functionality using test bench. Synthesize the design by setting proper constraints and obtain netlist. From the report generated identify the critical path, and maximum delay, total number of cells, power requirement and total area required.

**Tools required:**

- Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)
- Synthesis: Genus

**Full-Adder:** Full Adder is the adder which adds three inputs and produces two outputs. The first two inputs are a and b and the third input is an input carry as cin. The output carry is designated as cout and the normal output is sum.

**Full-Adder block diagram:**

 


**Full-Adder truth table:**

Inputs			Outputs	
a	b	cin	sum	cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

**4-bit Full Adder:** Binary adders are implemented to add two binary numbers. So in order to add two 4-bit binary numbers, we will need to use 4 full-adders. The 4 full-adders are

connected in cascade form. In this implementation, `cout` of each full-adder is connected to next `cin`.

**4-bit Full-Adder block diagram:**

 

**4-bit Full-Adder truth table:**

Inputs			Outputs	
a	b	cin	sum	cout
4'b0001	4'b1010	0	4'b1011	0
4'b1100	4'b1101		4'b1001	1
4'b0101	4'b1011		4'b0000	1
4'b1111	4'b1111		4'b1110	1
4'b0001	4'b1010	1	4'b1100	0
4'b1100	4'b1101		4'b1010	1
4'b0101	4'b1011		4'b0001	1
4'b1111	4'b1111		4'b1111	1

**Verilog code for 1-bit full-adder:**

```

module full_adder (a, b, cin, sum, cout);
input a, b, cin;
output sum, cout;

assign sum = a ^ b ^ cin;
assign cout = (a & b) | (cin & (a ^ b));

endmodule

```

**Verilog code for 4-bit full-adder:**

```
module four_bit_adder (a, b, cin, sum, cout);  
input [3:0] a, b;  
input cin;  
output [3:0] sum;  
output cout;
```

```
wire c1, c2, c3;
```

```
full_adder fa0 (a[0], b[0], cin, sum[0], c1);  
full_adder fa1 (a[1], b[1], c1, sum[1], c2);  
full_adder fa2 (a[2], b[2], c2, sum[2], c3);  
full_adder fa3 (a[3], b[3], c3, sum[3], cout);
```

```
endmodule
```

***Test bench for 4-bit full-adder:***

```
module test_adder;  
reg [3:0] a, b;  
reg cin;  
wire [3:0] sum;  
wire cout;
```

```
four_bit_adder f1 (a, b, cin, sum, cout);
```

```
initial  
begin  
$monitor ("time = %0d", $time, "ns", "a = %0b", a, "b = %0b", b, "cin = %0b", cin, "sum =  
%0b", sum, "cout = %0b", cout);  
#30 $finish;  
end
```


```
initial  
begin  
a = 4'b0011; b = 4'b0011; cin = 1'b0;  
#10; a = 4'b1011; b = 4'b1000; cin = 1'b1;  
#10; a = 4'b1111; b = 4'b1100; cin = 1'b1;
```

```
end
```


```
endmodule
```

**Result:**

Simulation:

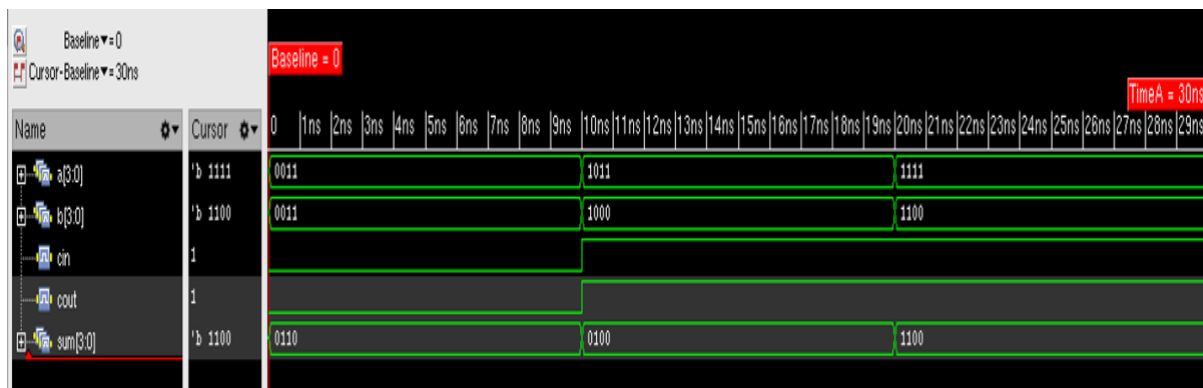

Schematic:

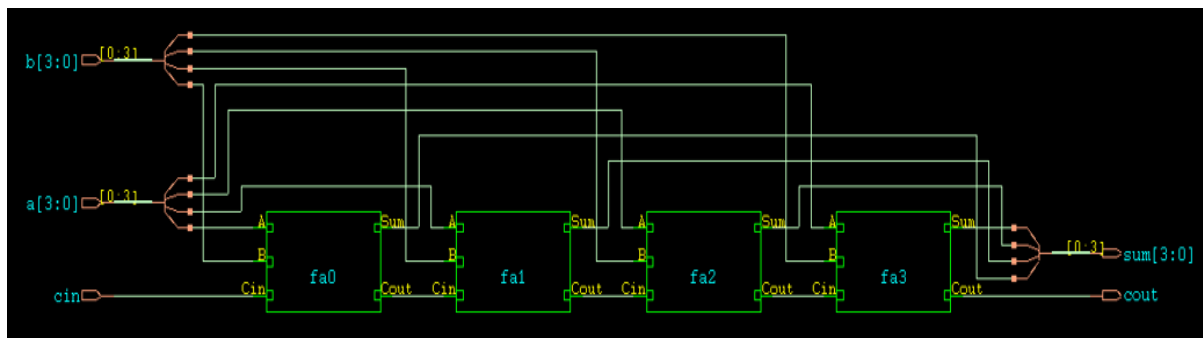

**Result:**

Non-GUI Output:

GUI Output:

Area Report

Power Report

Gates Report:

Timing Report:

Schematic:

7) Four bit Synchronous MOD-N counter with Asynchronous reset

\* Write Verilog Code

\* Verify functionality using Test-bench



- \* Synthesize the design targeting suitable library and by setting area and timing constraints
- \* Tabulate the Area, Power and Delay for the Synthesized netlist Identify Critical path

```
module modn_counter #(
    parameter MODULO = 10,
    parameter WIDTH = $clog2(MODULO) // Calculate the required bit-width
) (
    input wire clk,
    input wire rst,
    input wire en,
    output reg [WIDTH-1:0] count
);

always @(posedge clk or posedge rst) begin
    if (rst)
        count <= 0;
    else if (en) begin
        if (count == MODULO - 1)
            count <= 0;
        else
            count <= count + 1;
    end
end

endmodule
```

```
module tb_modn_counter;

    reg clk, rst, en;

    wire [3:0] count;

    modn_counter #(MODULO(10)) uut (
```

```
.clk(clk),
.rst(rst),
.en(en),
.count(count)
);
always #5 clk = ~clk;
initial begin
    clk = 0; rst = 1; en = 0;
    #10 rst = 0; en = 1;
    #100 $finish;
end
initial begin
    $monitor("Time: %t | Count: %d", $time, count);
end
endmodule
```

### Creating an SDC File:

- In terminal type “gedit constraints\_top.sdc” to create an SDC file. **(This file is common for all programs)**
- The SDC file must contain the following commands.

```
create_clock -name clk -period 2 -waveform {0 1} [get_ports "clk"]
```

```
set_input_delay -max 0.8 -clock clk [all_inputs]
set_output_delay -max 0.8 -clock clk [all_outputs]
```

```
set_input_transition 0.2 [all_inputs]
set_max_capacitance 30 [get_ports]
```

```
set_clock_transition -rise 0.1 [get_clocks "clk"]
set_clock_transition -fall 0.1 [get_clocks "clk"]
```

```
set_clock_uncertainty 0.01 [get_ports "clk"]
```

```
set_input_transition 0.12 [all_inputs]
set_load 0.15 [all_outputs]
```

*set\_max\_fanout 30.00 [current\_design]*

**Result:**

*Non-GUI Output:*

*GUI Output:*

*Area Report*

Power Report

Gates Report:


Timing Report:

Schematic:

**8.a) Capture the schematic of CMOS inverter with load capacitance of 0.1pF and set the widths of inverter with  $W_n = W_p$ ,  $W_n = 2W_p$ ,  $W_n = W_p/2$  and length at the selected technology. Carry out the following:**

- i) Set the input signal to a pulse with rise time, fall time of 1ns and pulse width of 10ns and time period of 20ns and plot the input voltage and output voltage of designed inverter?**

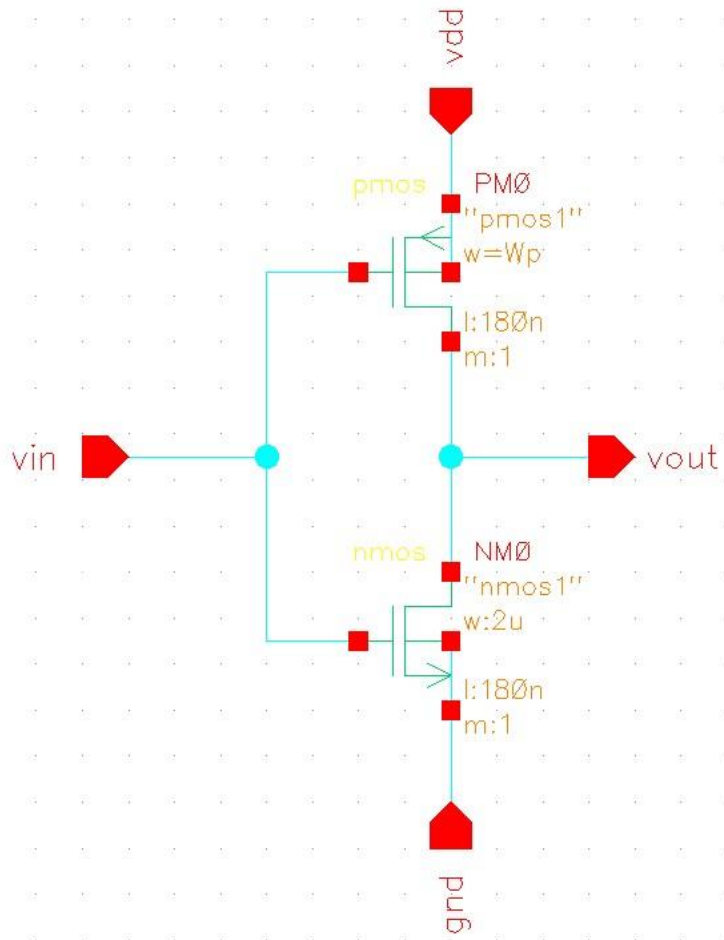
- ii) From the simulation result compute  $t_{pHL}$ ,  $t_{pLH}$  and  $t_d$  for all three geometrical settings of width?
- iii) Tabulate the results of delay and find the best geometry for minimum delay for CMOS inverter




CMOS Inverter schematic

Table of components for building the schematic:

Library Name	Cell Name	Properties
gpdk180	pmos	$W = Wp$ , $L = 180n$
gpdk180	nmos	$W = 2u$ , $L = 180n$

 

CMOS Inverter symbol

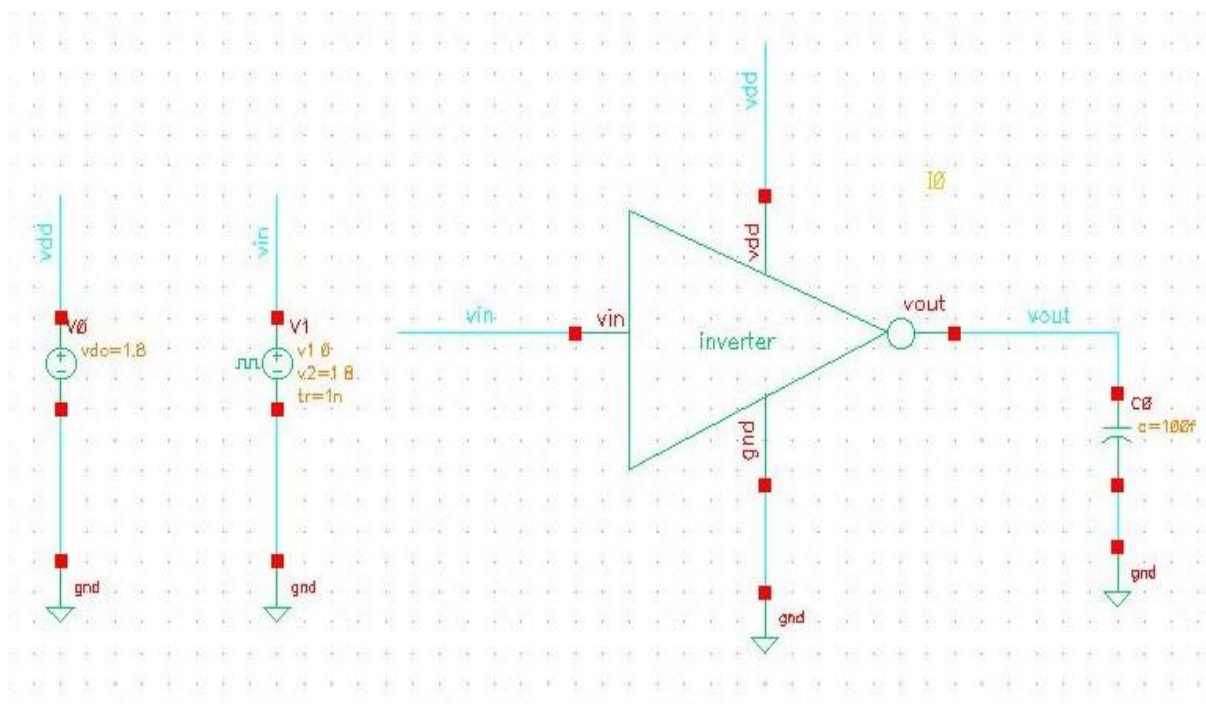

CMOS Inverter test schematic

**Table of components for building the test schematic:**

Library Name	Cell Name	Properties
analogLib	Vpulse	V1 = 0, V2 = 1.8, Period = 20n, Rise time = 1n, Fall time = 1n, Pulse width = 10n
analogLib	Vdc	Vdc = 1.8
analogLib	gnd	



analogLib	cap	0.1pF
-----------	-----	-------

**Table of values to setup for different analysis:**

Analysis Name	Settings	Properties
Transient	trans	Stop time = 100n, moderate
DC	<u>DC Analysis</u>	Save DC Operating point
	<u>Sweep Variable</u> Component Parameter	Component Name = Select input signal component (Vpulse) Parameter Name = dc
	<u>Sweep Range</u> Start – Stop	Start = 0, Stop 1.8

**Analog Simulation with spectre for inverter:**

*a) Transient Response*

*b) DC Response*


**Tabulated Values of Delays and DC Operating Points :****Values of  $t_{pHL}$ ,  $t_{pLH}$  and  $t_{pd}$  for different geometries**

Width setting	MOSFET	Width	$t_{pHL}$ (ps)	$t_{pLH}$ (ps)	$t_{pd}$ (ps)
$W_p = W_n$	pmos	2u			
	nmos	2u			
$W_p = W_n / 2$	pmos	1u			
	nmos	2u			
$W_p = 2 W_n$	pmos	4u			
	nmos	2u			

**DC operating point values for different geometries**

Width setting	MOSFET	Width	Vin (mV)	Vout (mV)
$W_p = W_n$	pmos	2u		
	nmos	2u		
$W_p = W_n / 2$	pmos	1u		
	nmos	2u		
$W_p = 2 W_n$	pmos	4u		
	nmos	2u		

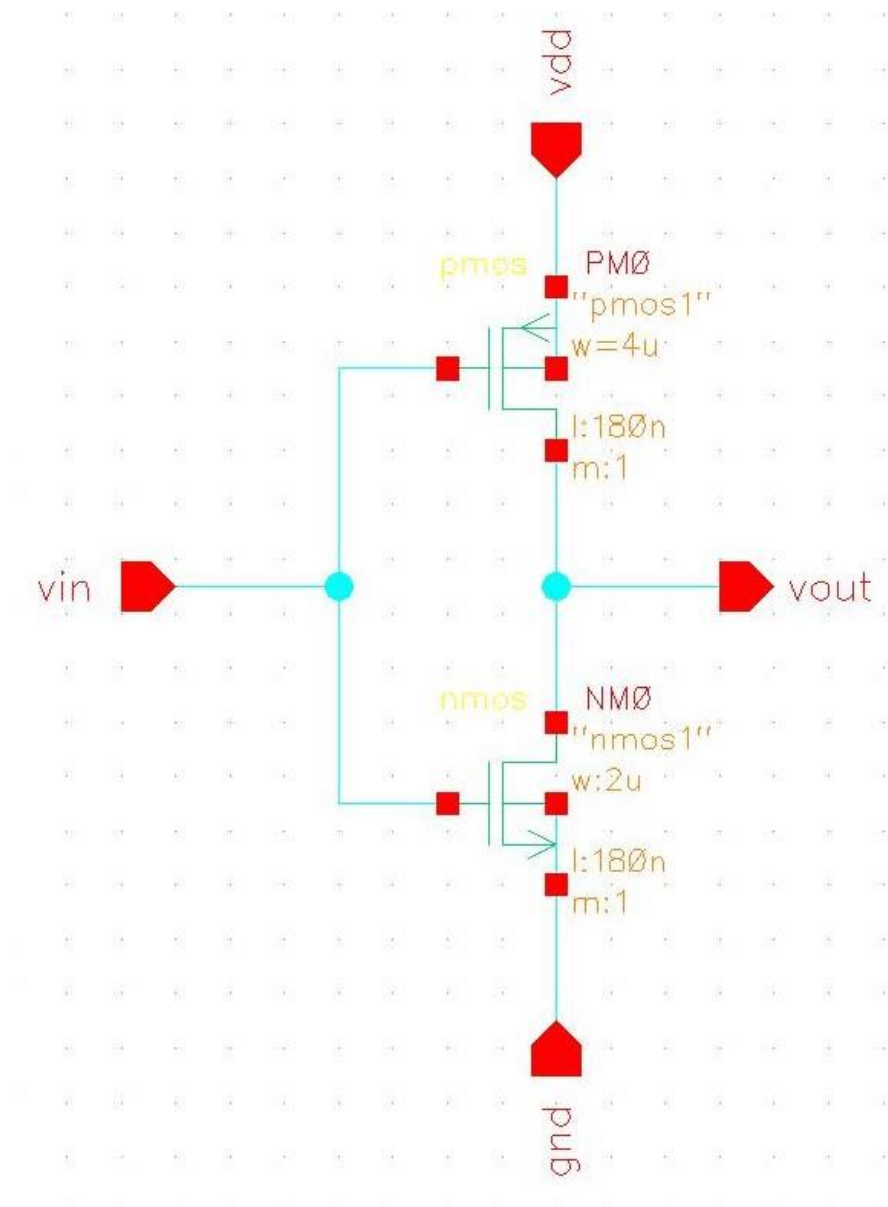
1. b) Draw layout of inverter with  $W_p/W_n = 40/20$ , use optimum layout methods. Verify for DRS and LVS, extract parasitic and perform post layout simulations, compare the results of with pre-layout simulations. Record the observations.




CMOS Inverter schematic

Table of components for building the schematic:

Library Name	Cell Name	Properties
gpd180	pmos	W = 4u, L = 180n
gpd180	nmos	W = 2u, L = 180n

 

CMOS Inverter symbol

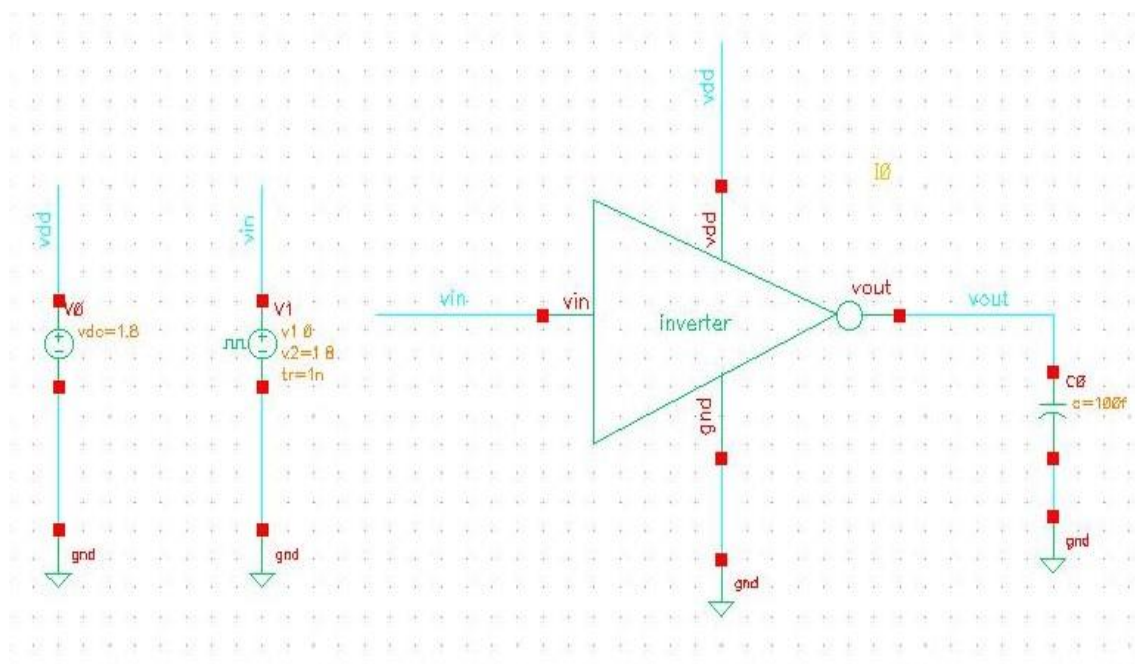

CMOS Inverter test schematic

Table of components for building the test schematic:


Library Name	Cell Name	Properties
analogLib	Vpulse	V1 = 0, V2 = 1.8, Period = 20n, Rise time = 1n, Fall time = 1n, Pulse width = 10n
analogLib	Vdc	Vdc = 1.8
analogLib	gnd	
analogLib	cap	0.1pF

**Analog Simulation with spectre for inverter test schematic:**

*a) Transient Response*


*b) DC Response*

**CMOS Inverter Layout:**

 

CMOS Inverter Layout

**CMOS Inverter av\_extracted view:**

 

CMOS Inverter av\_extracted view

**Analog Simulation with spectre for inverter layout:**

*a) Transient Response*

*b) DC Response*



**Tabulated Values of Delay:****Values of  $t_{phl}$ ,  $t_{plh}$  and  $t_{pd}$  for  $W_p/W_n = 40/20$** 


	$t_{phl}$ (ps)	$t_{plh}$ (ps)	$t_{pd}$ (ps)
<b>CMOS Inverter Test Schematic</b>			
<b>CMOS Inverter Layout</b>			

**DC operating point values for  $W_p/W_n = 40/20$** 

	$V_{in}$ (mV)	$V_{out}$ (mV)
<b>CMOS Inverter Test Schematic</b>		
<b>CMOS Inverter Layout</b>		

**9 a) Capture the schematic of 2-input CMOS NOR gate having similar delay as that of CMOS inverter computed in experiment above. Verify the functionality of**

 
**NOR gate and also find out the delay  $t_d$  for all four possible combinations of input vectors. Tabulate the result. Increase the drive strength to 2X and 4X and tabulate the result.**




Two Input CMOS NOR Gate schematic

**Table of components for building the schematic:**

Library Name	Cell Name	Properties
gpdk180	pmos	$W = W_p, L = 180n$
gpdk180	nmos	$W = W_n, L = 180n$

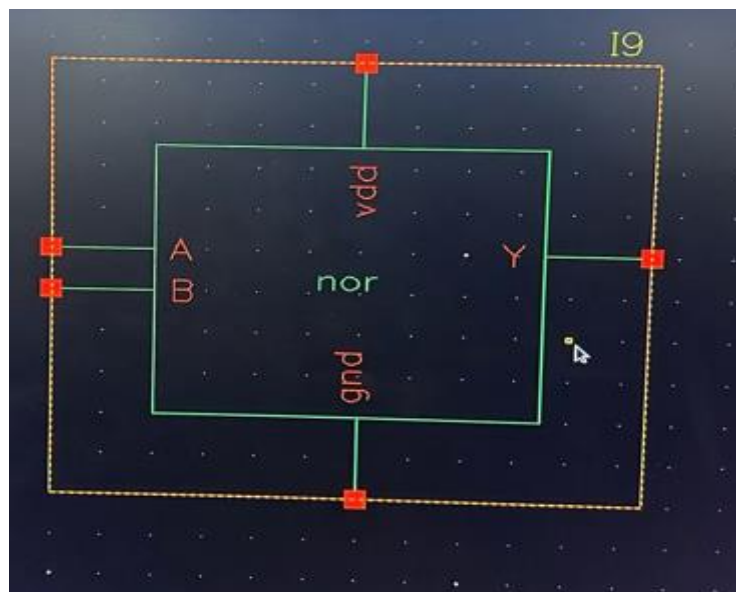

## Two Input CMOS NOR Gate symbol

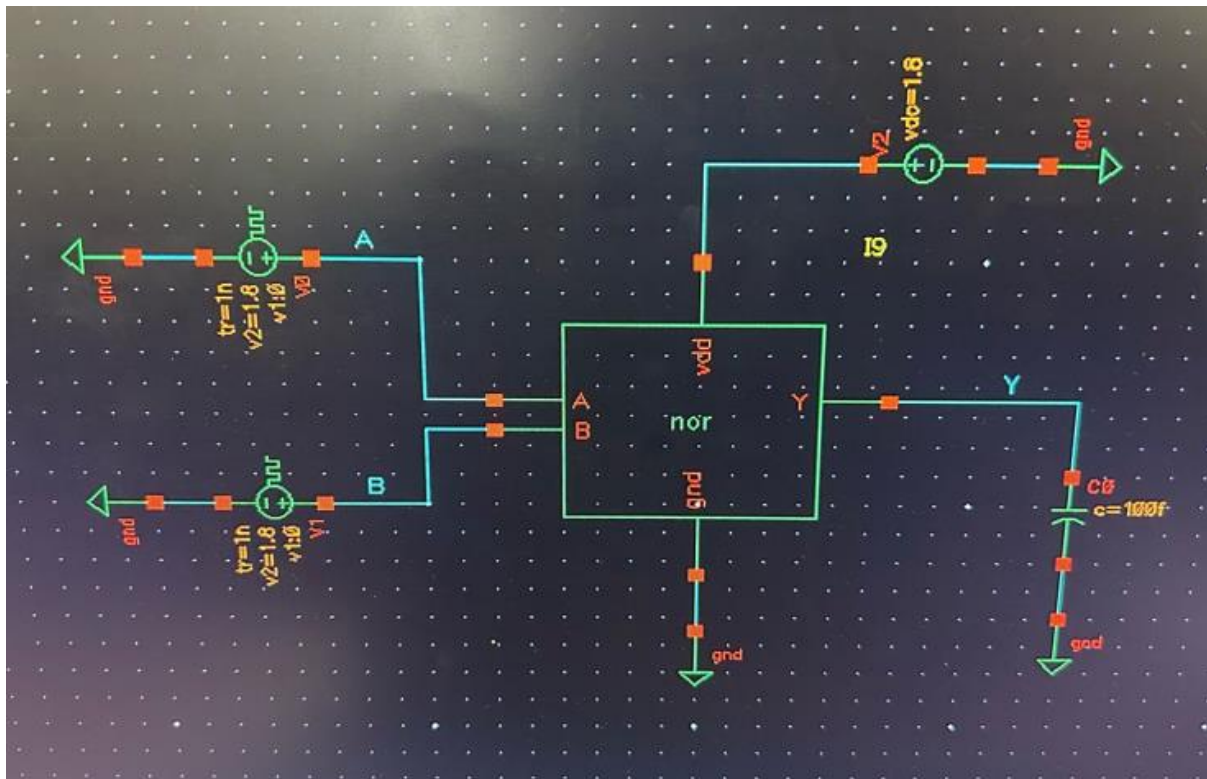

## Two Input CMOS NOR Gate test schematic

## Table of components for building the test schematic:

Library Name	Cell Name	Properties
analogLib	Vpulse	V1 = 0, V2 = 1.8, Period = 30n, Rise time = 1n, Fall time = 1n, Pulse width = 15n
analogLib	Vpulse	V1 = 0, V2 = 1.8, Period = 20n, Rise time = 1n, Fall time = 1n, Pulse width = 10n
analogLib	Vdc	Vdc = 1.8
analogLib	gnd	
analogLib	cap	0.1pF

## Table of values to setup for different analysis:

Analysis Name	Settings	Properties
---------------	----------	------------

Transient	trans	Stop time = 50n, moderate
-----------	-------	---------------------------

### Analog Simulation with spectre for Two Input CMOS NOR Gate:

#### a) Transient Response


### Tabulated Values of Delay:

#### Values of $t_{phl}$ , $t_{plh}$ and $t_{pd}$ for different geometries

MOSFET	Width	$t_{phl}$ (ps)	$t_{plh}$ (ps)	$t_{pd}$ (ps)
pmos	8u			
nmos	1u			
pmos	16u			
nmos	2u			
pmos	32u			
nmos	4u			

**10 a) Capture the schematic of Common Source Amplifier with PMOS Current Mirror load and find its transient response and AC response? Measure the Unity Gain Bandwidth (UGB), amplification factor by varying transistor geometries, study the impact of variation in width to UGB.**

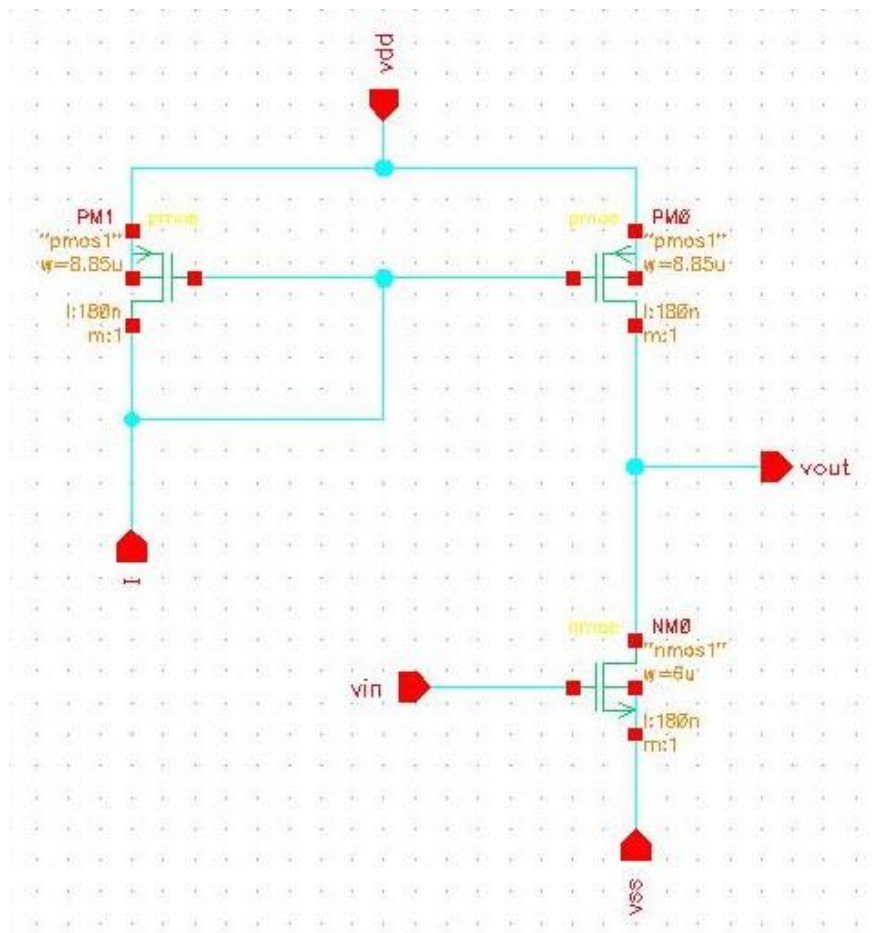
**b) Draw layout of common source amplifier, use optimum layout methods. Verify for DRS and LVS, extract parasitic and perform post layout simulations, compare the results of with pre-layout simulations. Record the observations.**




Common Source Amplifier schematic

Table of components for building the schematic:

Library Name	Cell Name	Properties
gpd180	pmos	W = 8.85u, L = 180n
gpd180	nmos	W = 6u, L = 180n

 

Common Source Amplifier symbol

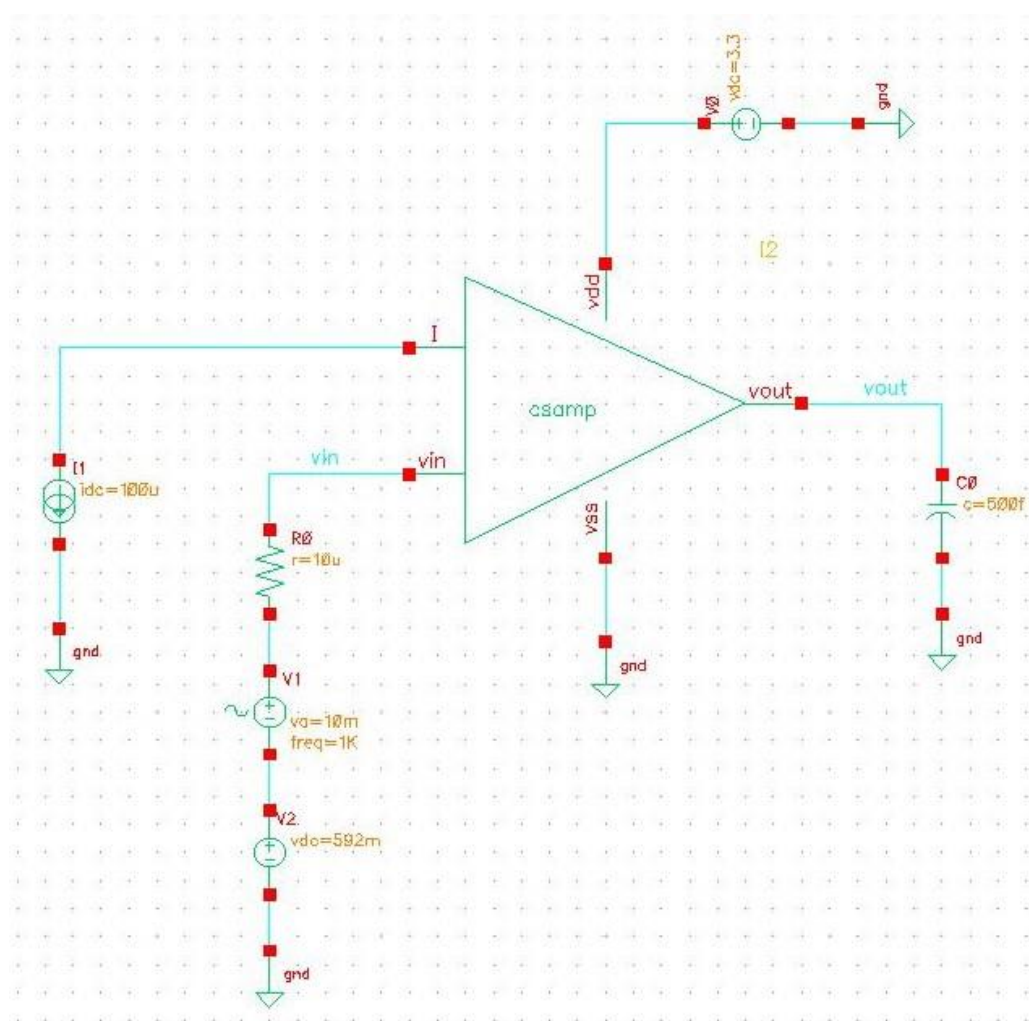

Common Source Amplifier test schematic



**Table of components for building the test schematic:**

Library Name	Cell Name	Properties
analogLib	Vdc	DC Voltage = 3.3 V ( $V_{dd}$ )
analogLib	Vsin	AC Magnitude = 1 V, Amplitude = 10u V, Frequency = 1K Hz
analogLib	Vdc	DC Voltage = 592m V
analogLib	res	Resistance = 10u Ohms
analogLib	idc	DC Current = 100u A
analogLib	cap	500f F

**Table of values to setup for different analysis:**


Analysis Name	Settings	Properties
Transient	trans	Stop time = 5m, moderate
DC	<u>DC Analysis</u>	Save DC Operating point
	<u>Sweep Variable</u> Component Parameter	Component Name = Select input signal component (Vpulse) Parameter Name = dc
	<u>Sweep Range</u> Start – Stop	Sweep Type = Linear Start = -5, Stop = 5, Step size = 10m V
AC	<u>Sweep Range</u> Start – Stop	Sweep Type = Logarithm, Start = 10, Stop = 10G, Points Per Decade = 10

**Analog Simulation with spectre for Common Source Amplifier:***a) Transient Response**b) DC Response*

*c) AC Response*


*d) AC Magnitude and Phase Response*

**Common Source Amplifier Layout:**

 

Common Source Amplifier Layout

 **Common Source Amplifier av\_extracted view:**



Common Source Amplifier av\_extracted view

**Analog Simulation with spectre for Common Source Amplifier:**

*a) Transient Response*

*b) DC Response*

*c) AC Response*

*d) AC Magnitude and Phase Response*


**Results:**

Common Source Amplifier		
	Gain	UGB
Schematic		
Layout		

**11 a) Construct the schematic of two-stage operational amplifier and measure the following:**

- i) UGB
- ii) dB bandwidth
- iii) Gain margin and phase margin with and without coupling capacitance
- iv) Use the op-amp in the inverting and non-inverting configuration and verify its functionality.
- v) Study the UGB, 3dB bandwidth, gain and power requirement in op-amp by varying the stage wise transistor geometries and record the observation.

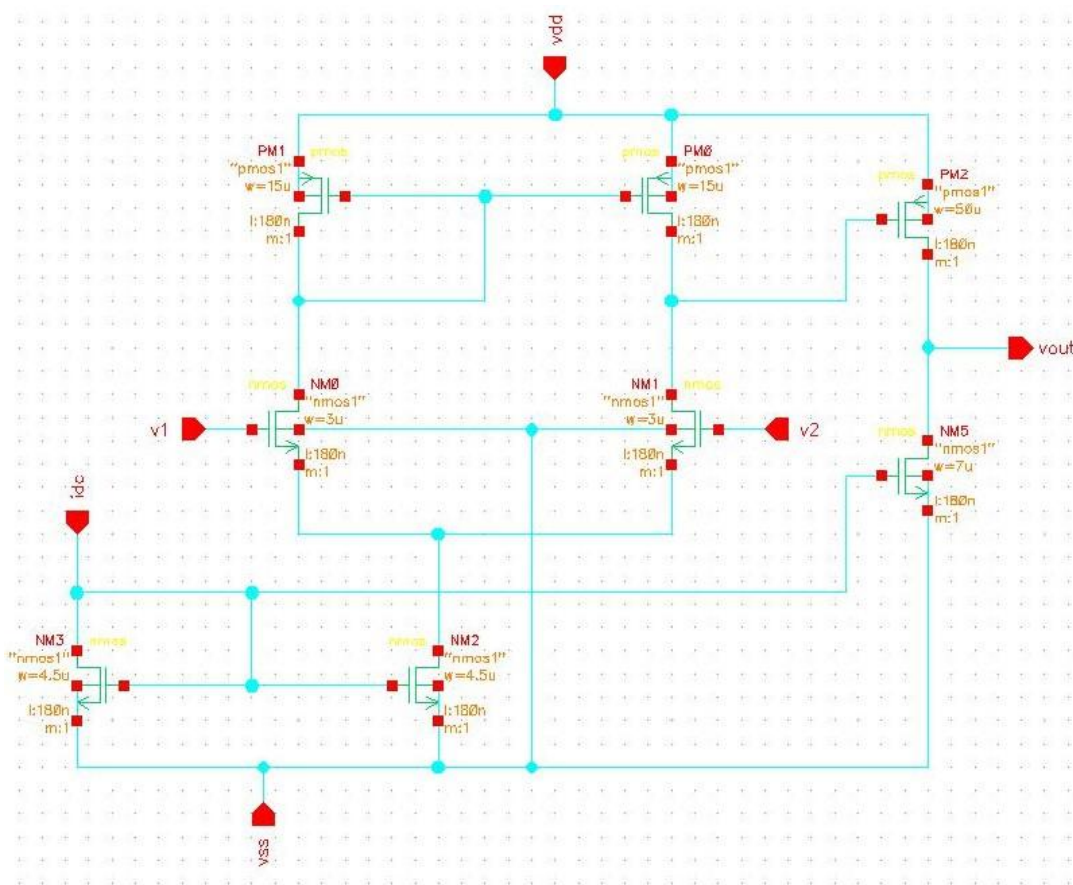b) Draw layout of two-stage operational amplifier with minimum transistor width set to 300 (in 180/90/45 nm technology), choose appropriate transistor geometries as per the results obtained in 11. a. Use optimum layout methods. Verify for DRS and LVS, extract parasitic and perform post layout simulations, compare the results of with pre-layout simulations. Record the observations.




Operational Amplifier schematic


Table of components for building the schematic:



Library Name	Cell Name	Properties
gpdk180	pmos	W = 15u, L = 180n W = 50u, L = 180n
gpdk180	nmos	W = 3u, L = 180n W = 4.5u, L = 180n W = 7u, L = 180n

 

Operational Amplifier symbol

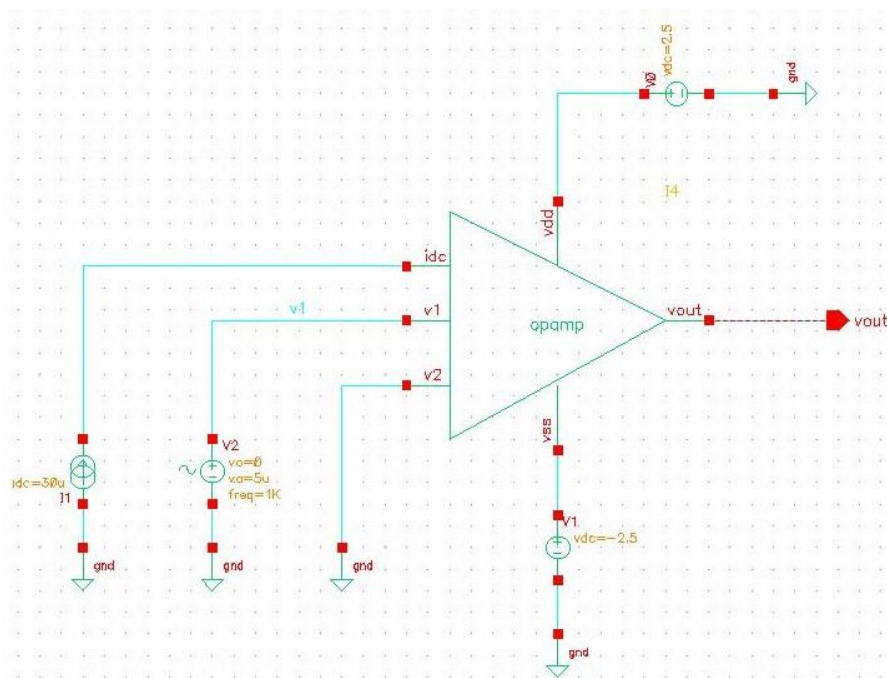

Operational Amplifier test schematic

**Table of components for building the test schematic:**

Library Name	Cell Name	Properties
analogLib	Vdc	DC Voltage = 2.5 V ( $V_{dd}$ ) DC Voltage = -2.5 V ( $V_{ss}$ )
analogLib	Vsin	AC Magnitude = 1 V, DC Voltage = 0 V, Offset Voltage = 0 V Amplitude = 5u V, Frequency = 1K Hz
analogLib	idc	DC Current = 30u A


**Table of values to setup for different analysis:**

Analysis Name	Settings	Properties
Transient	trans	Stop time = 5m, moderate
DC	<u>DC Analysis</u>	Save DC Operating point
	<u>Sweep Variable</u> Component Parameter	Component Name = Select input signal component (Vpulse) Parameter Name = dc
	<u>Sweep Range</u> Start – Stop	Start = -5, Stop = 5
AC	<u>Sweep Range</u> Start – Stop	Sweep Type = Automatic, Start = 100, Stop = 10G,

**Analog Simulation with spectre for Operational Amplifier:***a) Transient Response**b) DC Response*

*c) AC Response*

*d) AC Magnitude and Phase Response*

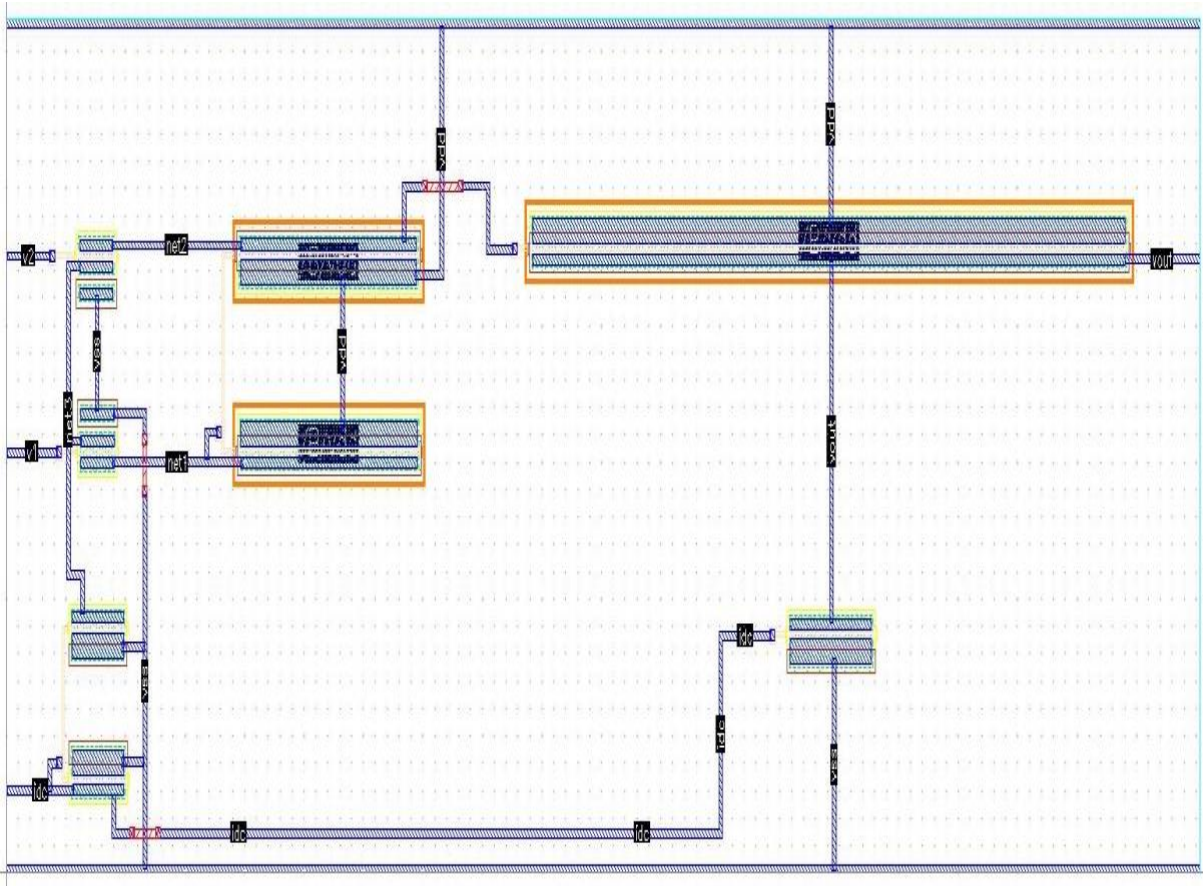**Operational Amplifier Layout:**

Operational Amplifier Layout

**Analog Simulation with spectre for Operational Amplifier:**

*a) Transient Response*

*b) DC Response*

*c) AC Response*

*d) AC Magnitude and Phase Response*

**Results:**

<b>Two-stage Operational Amplifier</b>
--


---

	Gain	UGB
Schematic		
Layout		

## DEMONSTRATION EXPERIMENTS (For CIE)

### 12 Design and characterize 6T binary SRAM cell and measure the following:

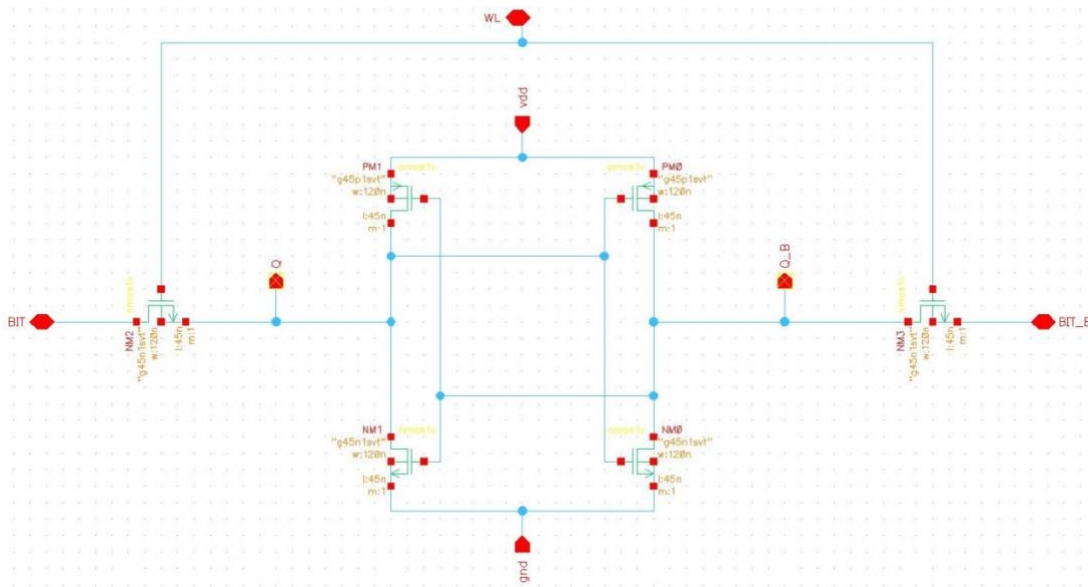
- i) Read Time, Write Time, SNM, Power
- ii) Draw Layout of 6T SRAM, use optimum layout methods. Verify for DRC & LVS, extract parasitic and perform post layout simulations, compare the results with pre-layout simulations. Record the observations.



6T binary SRAM cell schematic


Table of components for building the schematic:

Library Name	Cell Name	Properties
gpd45	pmos	W = 120n, L = 45n
gpd45	nmos	W = 120n, L = 45n

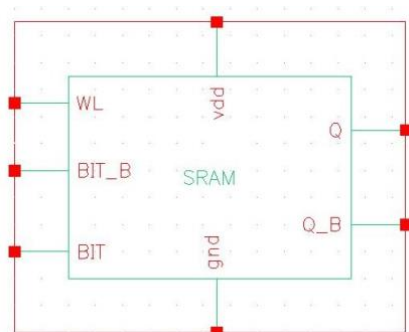

6T binary SRAM cell symbol



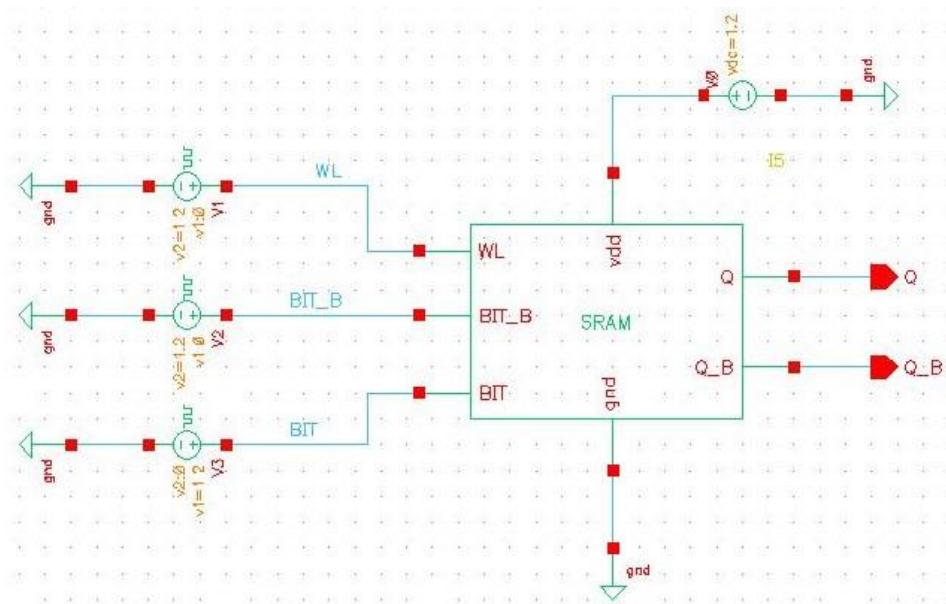

6T binary SRAM cell test schematic

Table of components for building the test schematic:

Library Name	Cell Name	Properties
analogLib	Vdc	DC Voltage = 1.2 V ( $V_{dd}$ )
analogLib	Vpulse	DC Voltage = 1.2 V, V1 = 0 V, V2 = 1.8, Period = 2n
analogLib	Vpulse	DC Voltage = 1.2 V, V1 = 1.2 V, V2 = 0, Period = 2n
analogLib	Vpulse	DC Voltage = 1.2 V, V1 = 0 V, V2 = 1.2, Period = 4n
analogLib	gnd	

Table of values to setup for different analysis:

Analysis Name	Settings	Properties
Transient	trans	Stop time = 8n, moderate
DC	<u>DC Analysis</u>	Save DC Operating point
	<u>Sweep Variable</u> Component Parameter	Component Name = Select input signal component (Vpulse) Parameter Name = dc
	<u>Sweep Range</u> Start – Stop	Start = 0, Stop = 1.2

**Analog Simulation with spectre for 6T binary SRAM cell:**

*a) Transient Response*

*b) DC Response*

*c) SNM*

*d) Power*

**Results:**

<b>6T binary SRAM cell</b>
----------------------------

---

Read Time	Write Time	SNM	Power

**13. Write verilog code for UART and carry out the following:**

- a. Verify the functionality using testbench.**
- b. Synthesize the design by setting area and timing constraints.**


- c. Tabulate the area, power and delay for the synthesized netlist, identified the critical path.

**Tools required:**

- Functional Simulation: Incisive Simulator (ncvlog, ncelab, ncsim)
- Synthesis: Genus

**UART:** A universal asynchronous receiver-transmitter (UART) is a peripheral device for asynchronous serial communication in which the data format and transmission speeds are configurable. It sends data bits one by one, from the least significant to the most significant, framed by start and stop bits so that precise timing is handled by the communication channel.

**UART Block diagram:**

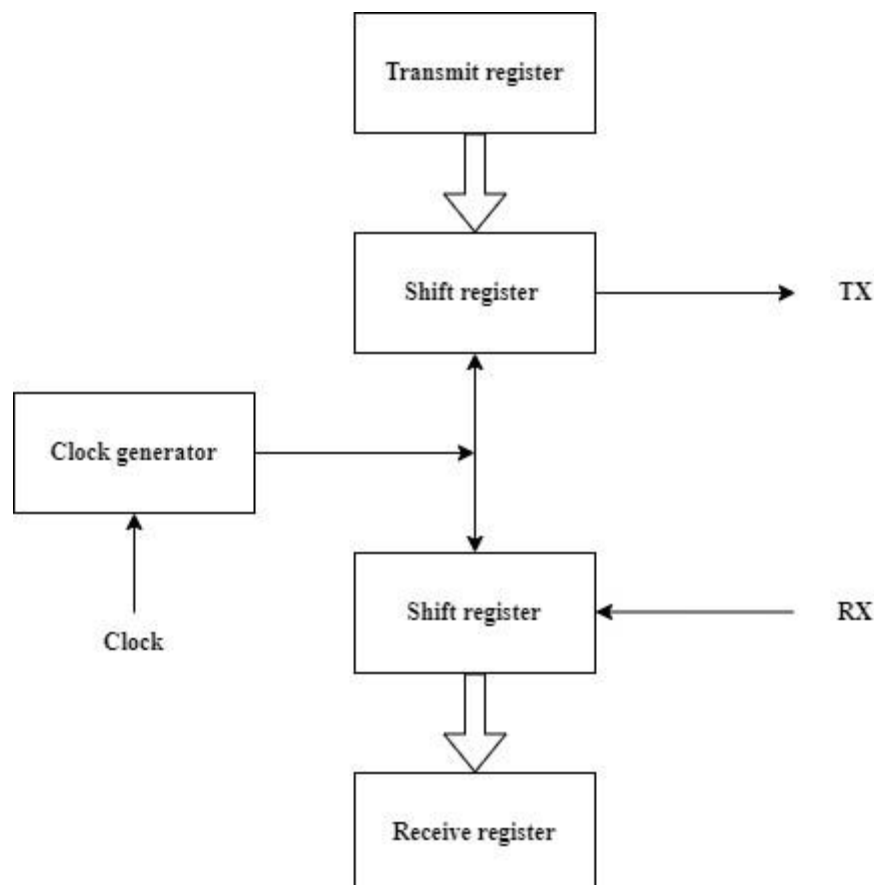

**Verilog code for UART:**

```
module uart_transmitter (input clk, input reset, input [7:0] data_in, output reg tx_out, output
reg tx_busy);
```

```
localparam IDLE = 2'b00;
```

```
localparam START_BIT = 2'b01;
```

```
localparam DATA_BITS = 2'b10;
```

```
localparam STOP_BIT = 2'b11;
```

```
reg state_t;
```

```
reg [2:0] state;
```

```
reg [3:0] bit_counter;
```

```
reg [7:0] transmit_data_reg;
```

```
parameter BAUD_RATE = 9600;
```

```
parameter CLOCK_FREQ = 50_000_000;
```

```
localparam BIT_CYCLES = CLOCK_FREQ / BAUD_RATE;
```

```
always @ (posedge clk or posedge reset) begin
```

```
if (reset) begin
```

```
state <= IDLE;
```

```
tx_busy <= 0;
```

```
bit_counter <= 0;
```

```
transmit_data_reg <= 8'b0;
```

```
end
```

```
else
```

```
begin
```

```
case (state)
```

```
IDLE: begin
```

```
tx_out <= 1;
```

```
if (tx_busy) begin
```

```
state <= START_BIT;
```

```
bit_counter <= 0;
```

```
end
```

```
end
```

```
START_BIT: begin
```

```
tx_out <= 0;
```

```
state <= DATA_BITS;
```

```
end
```

```
DATA_BITS: begin
```

```
tx_out <= transmit_data_reg[bit_counter];
```

```
bit_counter <= bit_counter + 1;
```

```
if (bit_counter == 7) begin
```

```
state <= STOP_BIT;
```

```
end
```

```
end
```

```
STOP_BIT: begin
```

```
tx_out <= 1;
```

```
state <= IDLE;
```

```
tx_busy <= 0;
```

```
end
```

```
endcase
```

```
end
```

```
end
```

```
always @ (posedge clk) begin
```

```
if (reset)
```

```
transmit_data_reg <= 8'b0;
```

```
else if (state == IDLE && !tx_busy)
```

```
transmit_data_reg <= data_in;
```

```
end
```

```
always @ (posedge clk) begin
```

```
if (!reset && !tx_busy && state == IDLE)
tx_busy <= 1;
end
endmodule

module uart_receiver (input clk, input reset, input rx_in, output reg [7:0] data_out,
output reg rx_ready);

localparam IDLE = 2'b00;
localparam START_BIT = 2'b01;
localparam DATA_BITS = 2'b10;
localparam STOP_BIT = 2'b11;

reg state_t;

reg [2:0] state;
reg [3:0] bit_counter;
reg [7:0] receive_data_reg;

parameter BAUD_RATE = 9600;
parameter CLOCK_FREQ = 50_000_000;
localparam BIT_CYCLES = CLOCK_FREQ / BAUD_RATE;
always @ (posedge clk or posedge reset) begin
if (reset) begin
state <= IDLE;
rx_ready <= 0;
bit_counter <= 0;
receive_data_reg <= 8'b0;
end
else
begin
case (state)
IDLE: begin
```



```
if (!rx_in) begin
state <= START_BIT;
bit_counter <= 0;
end
end
```

```
START_BIT: begin
state <= DATA_BITS;
end
```

```
DATA_BITS: begin
receive_data_reg[bit_counter] <= rx_in;
bit_counter <= bit_counter + 1;
if (bit_counter == 7) begin
state <= STOP_BIT;
end
end
```

```
STOP_BIT: begin
state <= IDLE;
rx_ready <= 1;
end
endcase
end
end
```

```
always @ (posedge clk) begin
if (reset)
data_out <= 8'b0;
else if (rx_ready)
data_out <= receive_data_reg;
end
endmodule
```

***Test bench for UART:***

```
module uart_tb;

parameter BAUD_RATE = 9600;
parameter CLOCK_FREQ = 50_000_000;

reg clk;
reg reset;
reg [7:0] data_in;
reg rx_in;

wire tx_out;
wire tx_busy;
wire [7:0] data_out;
wire rx_ready;

uart_transmitter  uart_tx  (.clk(clk),  .reset(reset),  .data_in(data_in),  .tx_out(tx_out),
.tx_busy(tx_busy));

uart_receiver  uart_rx  (.clk(clk),  .reset(reset),  .rx_in(rx_in),  .data_out(data_out),
.rx_ready(rx_ready));

always #5 clk = ~clk;

initial
begin
clk = 0;
reset = 1;
data_in = 8'b11011011;
#10 reset = 0;
#10 BAUD_RATE * 10;
```

```
#10 rx_in = 0;  
#10 rx_in = 1;  
#10 rx_in = 0;  
#10 rx_in = 1;  
#100 $finish;  
end  
endmodule
```

**Result:**

Non-GUI output:

GUI output:

Area report:

Power report:

Timing report:

Schematic:















